



INDEX

Sr. No.	Name of Experiment	D.O.P.	D.O.C.	Page No.	Remark
1	To verify the truth table of various logic gates using ICs.				
2	To realize the gates using universal gates.				
3	To realize half adder and full adder.				
4	Study of flip flop IC				
5	To implement ripple carry adder.				
6	To implement carry look ahead adder.				
7	To implement Booth's algorithm.				
8	To implement restoring division algorithm.				
9	To implement non restoring division algorithm.				
10	To implement ALU design.				



Experiment No. 1
Truth table of various logic gates using ICs.
Name: Ketan mahadik
Roll Number: 24
Date of Performance:
Date of Submission:

Aim - To verify the truth table of various logic gates using ICs.

Objective -

1. Understand how to use the breadboard to patch up, test your logic design and debug it.
2. The principal objective of this experiment is to fully understand the function and use of logic gates.
3. Understand how to implement simple circuits based on a schematic diagram using logic gates.

Components required -

1. IC's 7408, 7432, 7404
2. Bread Board.
3. Connecting wires.

Theory -

In digital electronics, a gate is logic circuits with one output and one or more inputs. Logic gates are available as integrated circuits.

AND gate :

AND gate performs logical multiplication, more commonly known as AND operation. The AND gate output will be in high state only when all the inputs are in high state. 7408 is a Quad 2 input AND gate.

OR gate:

It performs logical addition. Its output become high if any of the inputs is in logic high. 7432 is a Quad 2 input OR gate.

NOT gate:


It performs basic logic function for inversion or complementation. The purpose of the inverter is to change one logic level to the opposite level. IC 7404 is a Hex inverter.

Circuit Diagram, Truth Table -


AND Gate -




A	B	Y(A.B)
0	0	0
0	1	0
1	0	0
1	1	1

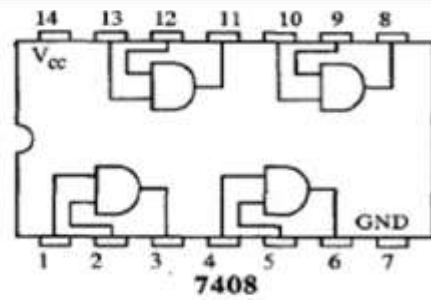


OR Gate -

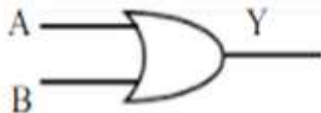


A	B	Y(A+B)
0	0	0
0	1	1
1	0	1
1	1	1

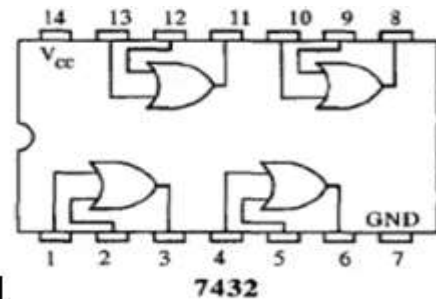

NOT Gate -

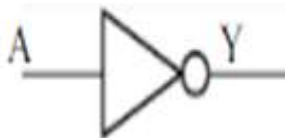

A	Y=A'
0	1
1	0

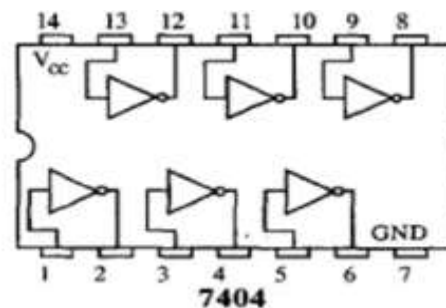


Screenshot:



Vidyavardhini's College of Engineering & Technology

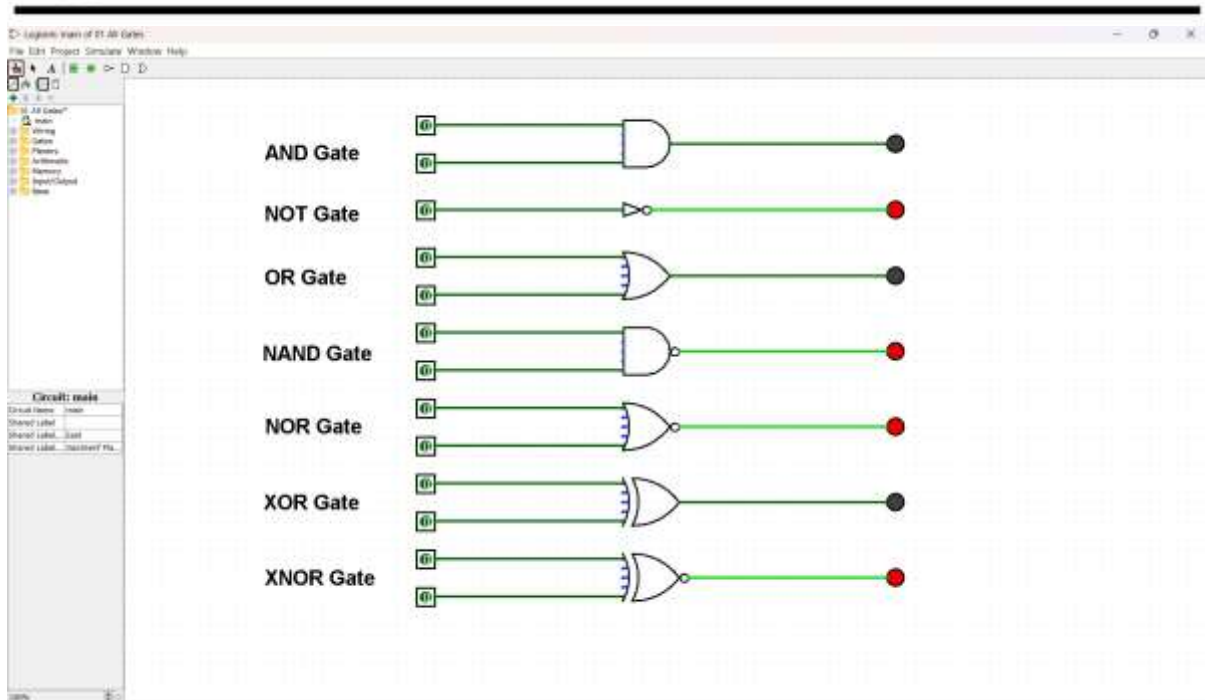Department of Artificial Intelligence and Data Science



Procedure:

1. Test all the components in the IC packages using a digital IC tester. Also assure whether all the connecting wires are in good condition by testing for the continuity using a Multimeter or a trainer kit.
2. Verify the dual in line package (DIP) in/out of the IC before feeding the inputs.
3. Set up the circuits and observe the outputs.

Conclusion -

Through this experiment, we aimed to showcase how these logic gates process binary input signals to produce specific output states, as outlined in their respective truth tables, by utilizing the logical behavior and functionality of the different types of gates, including AND, OR, NOT, NAND, NOR, and XOR gates.

This hands-on approach provided a practical understanding of fundamental digital logic principles and reinforced the relationship between logical operation and the resulting output, essentials for the further study and application in the field of digital electronics.



Experiment No. 2
Basic gates using universal gates.
Name: Ketan Mahadik
Roll Number: 24
Date of Performance:
Date of Submission:

Aim - To realize the gates using universal gates.

Objective -

- 1) To study the realization of basic gates using universal gates.
- 2) Understanding how to construct any combinational logic function using NAND or NOR gates only.

Theory -

AND, OR, NOT are called basic gates as their logical operation cannot be simplified further. NAND and NOR are called universal gates as using only NAND or only NOR, any logic function can be implemented.

Components required -


1. IC's 7400(NAND) 7402(NOR)
2. Bread Board.
3. Connecting wires.



Circuit Diagram -


Implementation using NAND gate:

(a) NOT gate: $Y = A'$

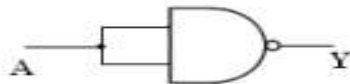


A	Y
0	1
1	0

(b) AND gate: $Y = A \cdot B$

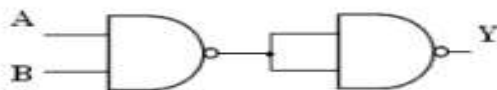


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

(c) OR gate: $Y = A + B$

 


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

(d) NOR gate: $Y = (A + B)'$

 

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

(e) Ex-OR gate: $Y = A \oplus B$

 

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0




Implementation using NOR gate:

(a) NOT gate: $Y = A'$




A	Y
0	1
1	0

(b) AND gate: $Y = A \cdot B$

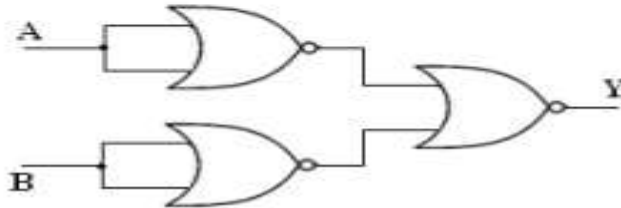


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

(c) OR gate: $Y = A + B$

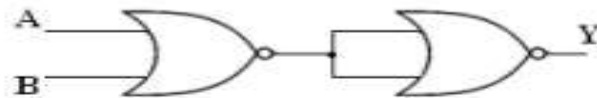


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

(d) NAND gate: $Y = (AB)'$

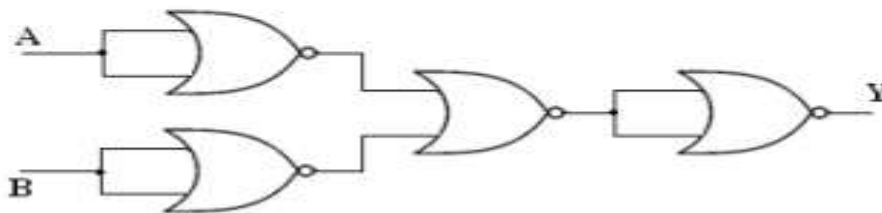

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

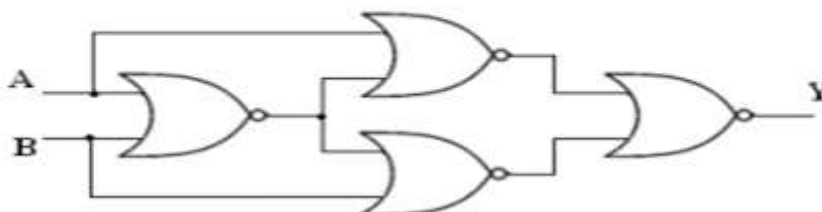(e) Ex-NOR gate: $Y = A \odot B = (A \oplus B)'$



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

Procedure:


- Connections are made as per the circuit diagrams.
- By applying the inputs, the outputs are observed and the operations are verified with the help of truth table.

Screenshot:



Vidyavardhini's College of Engineering & Technology

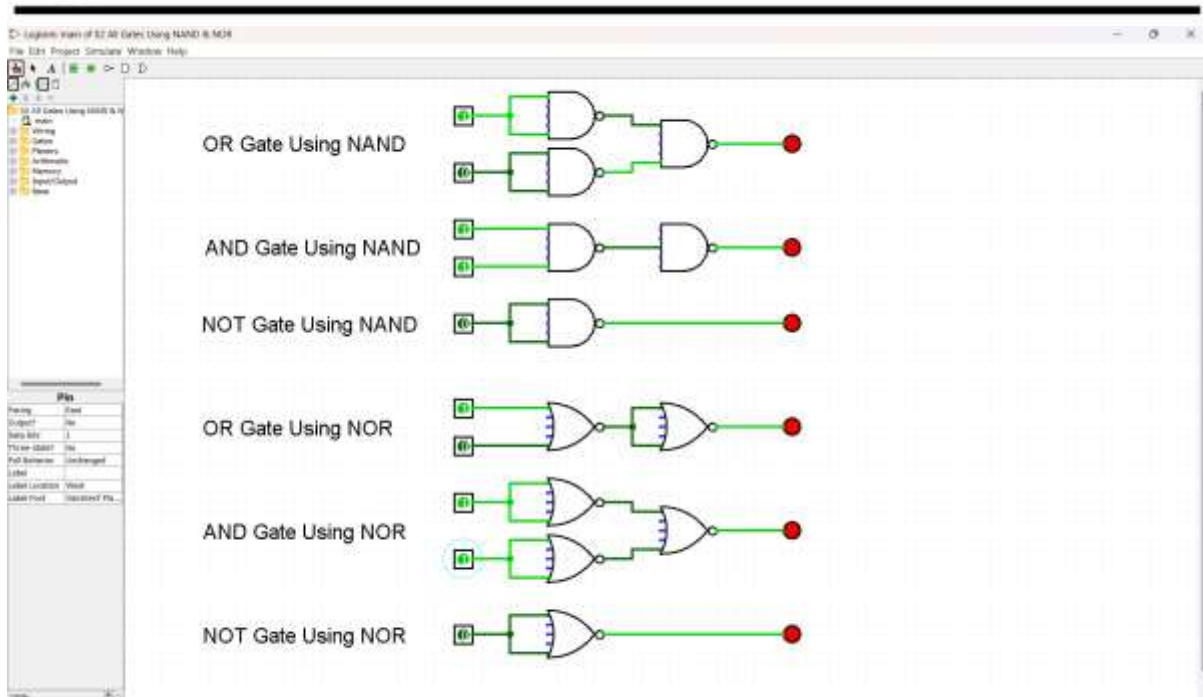Department of Artificial Intelligence and Data Science



Conclusion - - The experiment aimed to implement various logic gates using universal gates. By utilizing universal gates such as NAND or NOR, we successfully demonstrated their ability to simulate the behavior of AND, OR, NOT, and other gates. This experiment showcased the versatility and fundamental importance of universal gates in digital logic design, emphasizing their role in simplifying circuitry and facilitating the construction of complex logic functions using a minimal set of components.



Experiment No. 3
To realize half adder and full adder.
Name: Ketan mahadik
Roll Number: 24
Date of Performance:
Date of Submission:

Aim - To realize half adder and full adder.

Objective -

- 1) The objective of this experiment is to understand the function of Half-adder, Full-adder, Half-subtractor and Full-subtractor.
- 2) Understand how to implement Adder and Subtractor using logic gates.

Components required -

1. IC's - 7486(X-OR), 7432(OR), 7408(AND), 7404 (NOT)
2. Bread Board
3. Connecting wires.

Theory -

CSL302: Digital Logic & Computer Organization Architecture Lab



Vidyavardhini's College of Engineering & Technology

Department of Artificial Intelligence and Data Science

Half adder is a combinational logic circuit with two inputs and two outputs. The half adder circuit is designed to add two single bit binary numbers A and B. It is the basic building block for addition of two single bit numbers. This circuit has two outputs CARRY and SUM.

$$\text{Sum} = A \oplus B$$

$$\text{Carry} = A B$$

Full adder is a combinational logic circuit with three inputs and two outputs. Full adder is developed to overcome the drawback of HALF ADDER circuit. It can add two one bit numbers A and B. The full adder has three inputs A, B, and CARRY in, the circuit has two outputs CARRY out and SUM.

$$\text{Sum} = (A \oplus B) \oplus \text{Cin}$$

$$\text{Carry} = AB + \text{Cin}(A \oplus B)$$

Subtracting a single-bit binary value B from another A (i.e. A - B) produces a difference bit D and a borrow out bit B-out. This operation is called half subtraction and the circuit to realize it is called a half subtractor. The Boolean functions describing the half- Subtractor are

$$\text{Sum} = A \oplus B$$

$$\text{Carry} = A' B$$


Subtracting two single-bit binary values, B, Cin from a single-bit value A produces a difference bit D and a borrow out Br bit. This is called full subtraction. The Boolean functions describing the full-subtractor are

$$\text{Difference} = (A \oplus B) \oplus \text{Cin}$$

$$\text{Borrow} = A' B + A'(\text{Cin}) + B(\text{Cin})$$


Circuit Diagram and Truth Table -

Half-adder

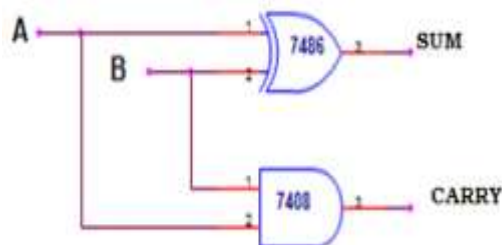

A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Full-adder

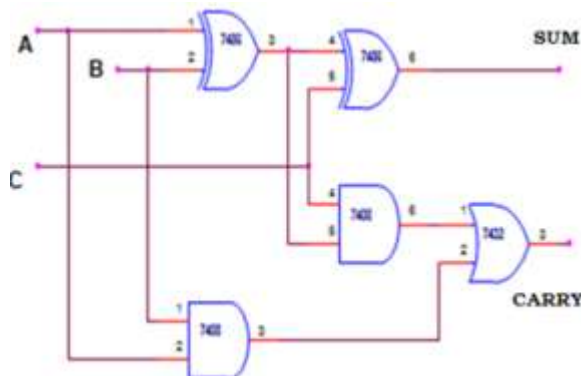

A	B	C	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Procedure -

1. Verify the gates.
2. Make the connections as per the circuit diagram.




Vidyavardhini's College of Engineering & Technology

Department of Artificial Intelligence and Data Science

3. Switch on VCC and apply various combinations of input according to truth table.
4. Note down the output readings for half/full adder and half/full subtractor, Sum/difference and the carry/borrow bit for different combinations of inputs verify their truth tables.

Screenshot:

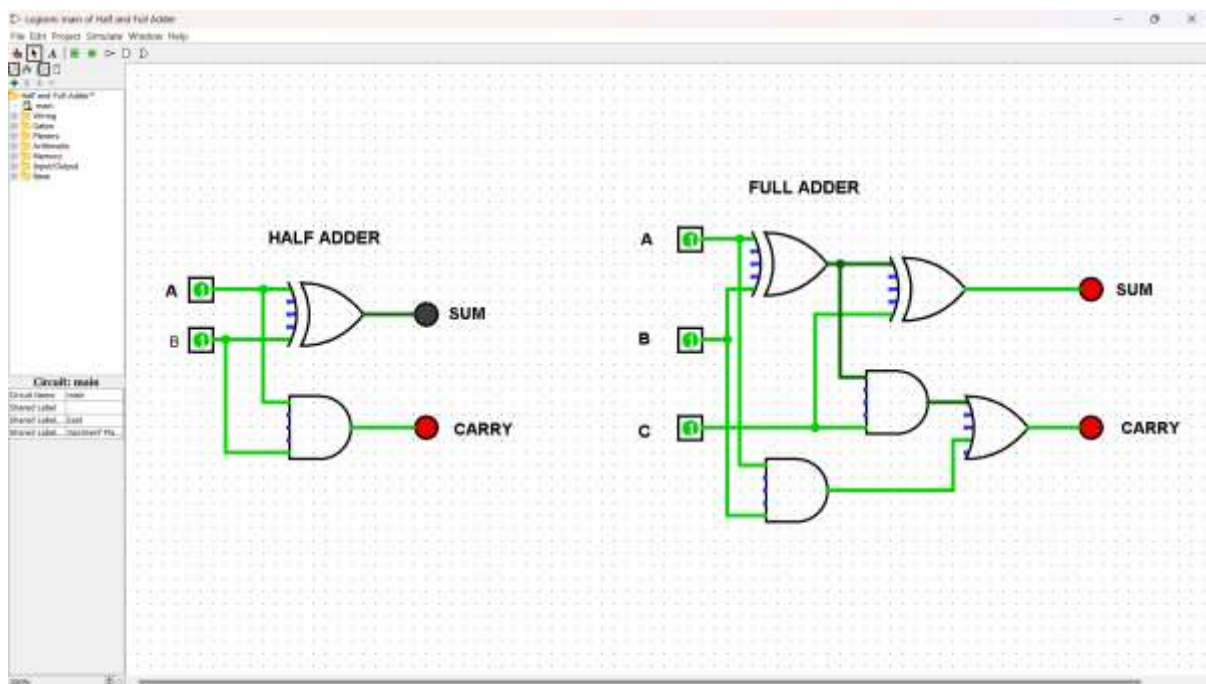

Conclusion - The experiment aimed to implement both a half adder and a full adder. Through this, we successfully showcased the fundamental building blocks of binary addition in digital circuits. The half adder provided the foundation for adding two binary digits, while the full adder extended this concept to handle three inputs, enabling more comprehensive binary addition. This experiment



Vidyavardhini's College of Engineering & Technology

Department of Artificial Intelligence and Data Science

Experiment No. 4
Study of flip flop IC
Name: Ketan mahadik
Roll Number: 29
Date of Performance:
Date of Submission:

Aim : Study of Flip Flop IC.

Objective : **Objective:** This experiment aims to understand the functioning of Flip Flop Integrated Circuits (ICs). It involves studying different types of Flip Flops, analyzing signal propagation, examining clock signal effects, observing state transitions, interpreting timing diagrams, comparing Flip Flop types, implementing logic circuits, troubleshooting, and recording/analyzing data.

Theory : Flip Flop ICs (Integrated Circuits) are fundamental building blocks in digital electronics used for storing and manipulating binary information. They are crucial components in digital circuits and are widely used in various applications such as memory units, counters, registers, and more. Flip Flops serve as basic storage elements in digital systems, allowing for the storage and transfer of binary information in the form of 0s and 1s.

There are several types of Flip Flops, each with its unique characteristics and applications. Some common types include D Flip Flop, JK Flip Flop, T Flip Flop, and SR Flip Flop. These Flip
CSL302: Digital Logic & Computer Organization Architecture Lab



Flops can be constructed using various logic gates, such as NAND gates, NOR gates, or a combination of gates.

1. D Flip Flop (Data Flip Flop):

Basic storage element that holds one data bit.

Transfers data to the output on clock signal transition.

Useful for edge-triggered synchronization.

Examples: 74HC74, CD4013.

2. JK Flip Flop:

Combines the features of the SR and D Flip Flops.

Allows toggling of output on certain conditions.

J and K inputs determine the behavior.

Examples: 74HC107, CD4027.

3. T Flip Flop (Toggle Flip Flop):

Toggles its output on each clock signal transition when T input is high.

Useful for frequency division and counters.

Examples: 74HC73, CD4013.

4. SR Flip Flop (Set-Reset Flip Flop):

Has set (S) and reset (R) inputs to control the outputs.

Output depends on the combination of S and R inputs.

Commonly used in asynchronous systems.



Examples: 74HC279, CD4043.

Conclusion : :- In conclusion, this experiment has not only enhanced our theoretical understanding of flip-flop operation but also provided hands-on experience in working with essential digital logic components. As we move forward in our study of digital electronics, these insights will serve as a solid foundation for more advanced projects and applications.

Experiment No. 5
Implement ripple carry adder
Name: Ketan mahadik
Roll Number: 24
Date of Performance:
Date of Submission:

Aim: To implement ripple carry adder.

Objective: To understand the operation of a ripple carry adder, specifically how the carry ripples through the adder.


1. examining the behavior of the working module to understand how the carry ripples through the adder stages
2. to design a ripple carry adder using full adders to mimic the behavior of the working module
3. the adder will add two 4 bit numbers

Theory: Arithmetic operations like addition, subtraction, multiplication, division are basic operations to be implemented in digital computers using basic gates like AND, OR, NOR, NAND etc. Among all the arithmetic operations if we can implement addition then it is easy to perform multiplication (by repeated addition), subtraction (by negating one operand) or division (repeated subtraction).

Half Adders can be used to add two one bit binary numbers. It is also possible to create a logical circuit using multiple full adders to add N-bit binary numbers. Each full adder inputs a Cin, which is the Cout of the previous adder. This kind of adder is a Ripple Carry Adder, since each carry bit "ripples" to the next full adder. The first (and only the first) full adder may be replaced



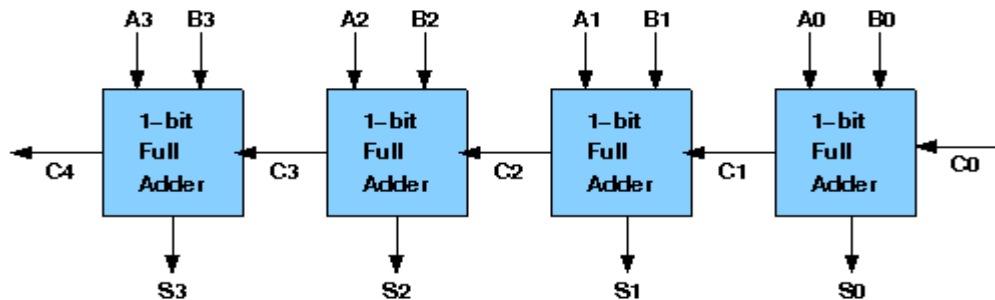by a half adder. The block diagram of 4-bit Ripple Carry Adder is shown here below -



The layout of ripple carry adder is simple, which allows for fast design time; however, the ripple carry adder is relatively slow, since each full adder must wait for the carry bit to be calculated from the previous full adder. The gate delay can easily be calculated by inspection of the full adder circuit. Each full adder requires three levels of logic. In a 32-bit [ripple carry] adder, there are 32 full adders, so the critical path (worst case) delay is $31 * 2(\text{for carry propagation}) + 3(\text{for sum}) = 65$ gate delays.

Design Issues:

The corresponding Boolean expressions are given here to construct a ripple carry adder. In the half adder circuit the sum and carry bits are defined as

$$\text{sum} = A \oplus B$$

$$\text{carry} = AB$$

In the full adder circuit the the Sum and Carry output is defined by inputs A, B and Carryin as
 $\text{Sum} = ABC + \bar{A}BC + A\bar{B}C + A\bar{B}\bar{C}$

$$\text{Carry} = ABC + \bar{A}BC + A\bar{B}C + A\bar{B}\bar{C}$$

Having these we could design the circuit. But, we first check to see if there are any logically equivalent statements that would lead to a more structured equivalent circuit.

With a little algebraic manipulation, one can see that

$$\begin{aligned} \text{Sum} &= ABC + \bar{A}BC + A\bar{B}C + A\bar{B}\bar{C} \\ &= (AB + \bar{A}B)C + (A\bar{B} + A\bar{B})\bar{C} \\ &= (A \oplus B)C + (A \oplus B)\bar{C} \\ &= A \oplus B \oplus C \end{aligned}$$

$$\begin{aligned} \text{Carry} &= ABC + \bar{A}BC + A\bar{B}C + A\bar{B}\bar{C} \\ &= AB + (\bar{A} + \bar{B})C \\ &= AB + (A \oplus B)C \end{aligned}$$

Procedure:

Procedure to perform the experiment: Design of Ripple Carry Adders


- 1) Start the simulator as directed. This simulator supports 5-valued logic.
- 2) To design the circuit we need 3 full adder, 1 half adder, 8 Bit switch(to give input), 3 Digital display(2 for seeing input and 1 for seeing output sum), 1 Bit display(to see the carry output), wires.
- 3) The pin configuration of a component is shown whenever the mouse is hovered on any



canned component of the palette or presses the 'show pin config' button. Pin numbering starts from 1 and from the bottom left corner (indicating with the circle) and increases anticlockwise.

- 4) For half adder input is in pin-5,8 output sum is in pin-4 and carry is pin-1, For full adder input is in pin-5,6,8 output sum is in pin-4 and carry is pin-1
- 5) Click on the half adder component(in the Adder drawer in the pallet) and then click on the position of the editor window where you want to add the component(no drag and drop, simple click will serve the purpose), likewise add 3 full adders(from the Adder drawer in the pallet), 8 Bit switches, 3 digital display and 1 bit Displays(from Display and Input drawer of the pallet, if it is not seen scroll down in the drawer)
- 6) To connect any two components select the Connection menu of Palette, and then click on the Source terminal and click on the target terminal. According to the circuit diagram connect all the components, connect 4 bit switches to the 4 terminals of a digital display and another set of 4 bit switches to the 4 terminals of another digital display. connect the pin-1 of the full adder which will give the final carry output. connect the sum(pin-4) of all the adders to the terminals of the third digital display(according to the circuit diagram shown in screenshot). After the connection is over click the selection tool in the pallet.
- 7) To see the circuit working, click on the Selection tool in the pallet then give input by double clicking on the bit switch, (let it be 0011(3) and 0111(7)) you will see the output on the output(10) digital display as sum and 0 as carry in bit display.

Circuit diagram of Ripple Carry Adder:

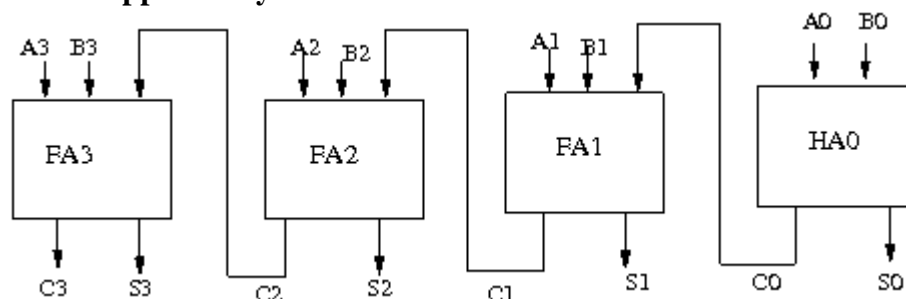

Components required:

The components needed to create 4 bit ripple carry adder is listed here -


- 4 full-adders
- wires to connect
- LED display to obtain the output

OR we can use

- 3 full-adders
- 1 half adder
- wires to connect
- LED display to obtain the output



Screenshots of Ripple Carry Adder:

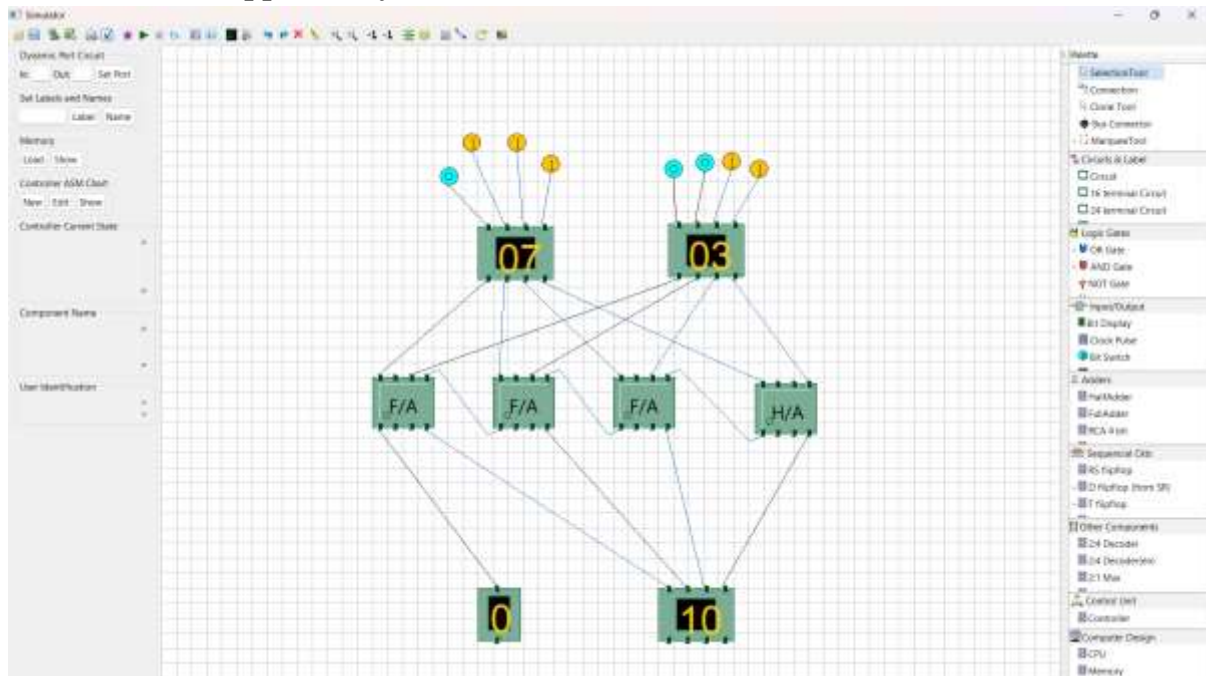

Conclusion: The aim of the experiment is to design and implement a ripple carry adder, a fundamental digital arithmetic circuit, to perform addition of binary numbers in a sequential and cascading manner.



Experiment No.6
Implement Carry Look Ahead Adder.
Name: Ketan mahadik
Roll Number: 24
Date of Performance:
Date of Submission:

Aim: . To implement carry look ahead adder.


Objective:

It computes the carries parallelly thus greatly speeding up the computation.

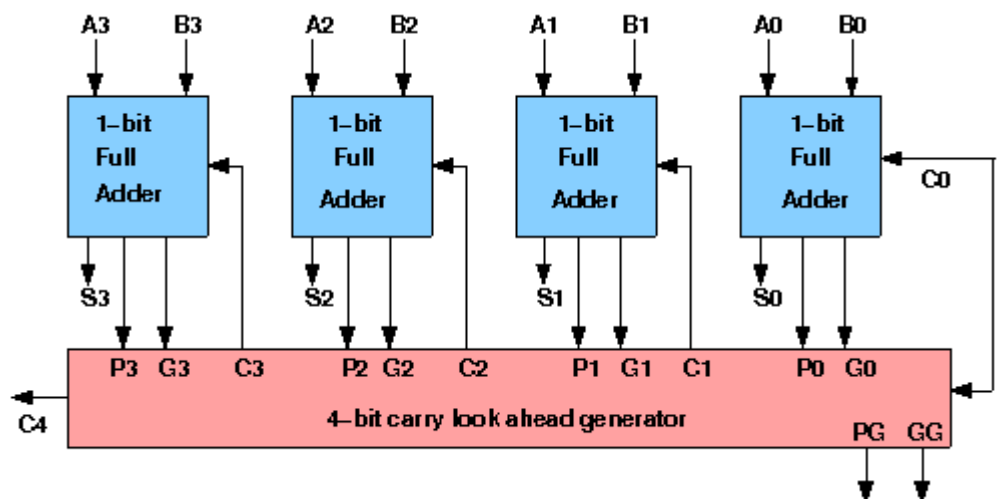1. To understanding behaviour of carry lookahead adder from module designed by the student as part of the experiment
2. To understand the concept of reducing computation time with respect of ripple carry adder by using carry generate and propagate functions.
3. The adder will add two 4 bit numbers

Theory:

To reduce the computation time, there are faster ways to add two binary numbers by using carry lookahead adders. They work by creating two signals P and G known to be Carry Propagator and Carry Generator. The carry propagator is propagated to the next level whereas the carry generator is used to generate the output carry ,regardless of input carry. The block diagram of a 4-bit Carry Lookahead Adder is shown here below -





The number of gate levels for the carry propagation can be found from the circuit of full adder. The signal from input carry C_{in} to output carry C_{out} requires an AND gate and an OR gate, which constitutes two gate levels. So if there are four full adders in the parallel adder, the output carry C_5 would have $2 \times 4 = 8$ gate levels from C_1 to C_5 . For an n -bit parallel adder, there are $2n$ gate levels to propagate through.

Design Issues :

The corresponding boolean expressions are given here to construct a carry lookahead adder. In the carry-lookahead circuit we need to generate the two signals carry propagator(P) and carry generator(G),

$$P_i = A_i \oplus B_i$$

$$G_i = A_i \cdot B_i$$

The output sum and carry can be expressed as

$$S_{mi} = P_i \oplus C_i$$

$$C_{i+1} = G_i + (P_i \cdot C_i)$$

Having these we could design the circuit. We can now write the Boolean function for the carry output of each stage and substitute for each C_i its value from the previous equations:

$$C_1 = G_0 + P_0 \cdot C_0$$

$$C_2 = G_1 + P_1 \cdot C_1 = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot C_0$$

$$C_3 = G_2 + P_2 \cdot C_2 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot C_0$$

$$C_4 = G_3 + P_3 \cdot C_3 = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot C_0$$

Procedure:

Procedure to perform the experiment: Design of Carry Look ahead Adders


- 1) Start the simulator as directed. This simulator supports 5-valued logic.
- 2) To design the circuit we need 7 half adder, 3 OR gate, 1 V+(to give 1 as input), 3 Digital display(2 for seeing input and 1 for seeing output sum), 1 Bit display(to see the carry output), wires.
- 3) The pin configurations of a component are shown whenever the mouse is hovered on any canned component of the palette or press the 'show pinconfig' button. Pin numbering starts from 1 and from the bottom left corner (indicating with the circle) and increases anticlockwise.
- 4) For half adder input is in pin-5,8 output sum is in pin-4 and carry is pin-1
- 5) Click on the half adder component(in the Adder drawer in the pallet) and then click on the position of the editor window where you want to add the component(no drag and drop, simple click will serve the purpose), likewise add 6 more full adders(from the Adder drawer in the pallet), 3 OR gates(from Logic Gates drawer in the pallet), 1 V+, 3 digital display and 1 bit Displays(from Display and Input drawer of the pallet, if it is not seen scroll down in the drawer)
- 6) To connect any two components select the Connection menu of Palette, and then click on the Source terminal and click on the target terminal. According to the circuit diagram



connect all the components; connect V+ to the upper input terminals of 2 digital displays according to you input. Connect the OR gates according to the diagram shown in the screenshot connect the pin-1 of the half adder which will give the final carry output. Connect the sum (pin-4) of those adders to the terminals of the third digital display which will give output sum. After the connection is over click the selection tool in the pallet.

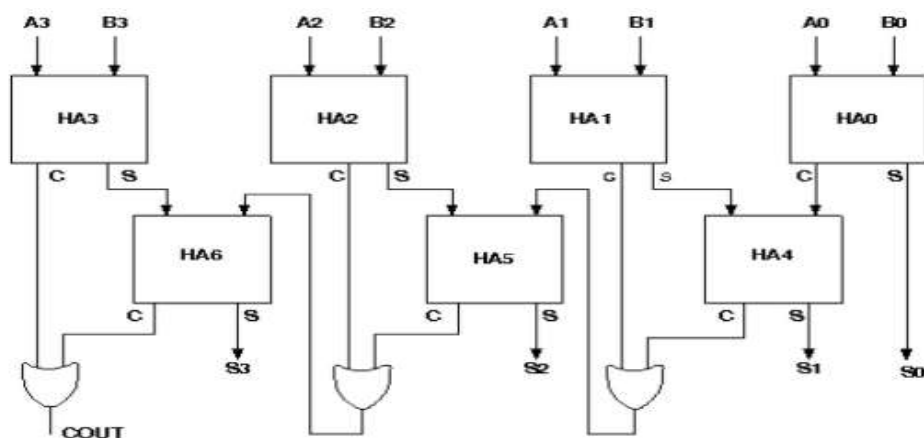- 7) See the output; in the screenshot diagram we have given the value 0011(3) and 0111(7) so get 10 as sum and 0 as carry. You can also use many bit switches instead of V+ to give input and by double clicking those bit switches can give different values and check the result.

Circuit diagram of Carry Look Ahead Adder:




Components required:

The components needed to create 4 bit carry look ahead adder is listed here -

1. 7 half-adders: 4 to create the look adder circuit, and 3 to evaluate S_i and $P_i \cdot C_i$
2. 3 OR gates to generate the next level carry C_{i+1}
3. wires to connect
4. LED display to obtain the output



Screenshots of Carry Look Ahead Adder:

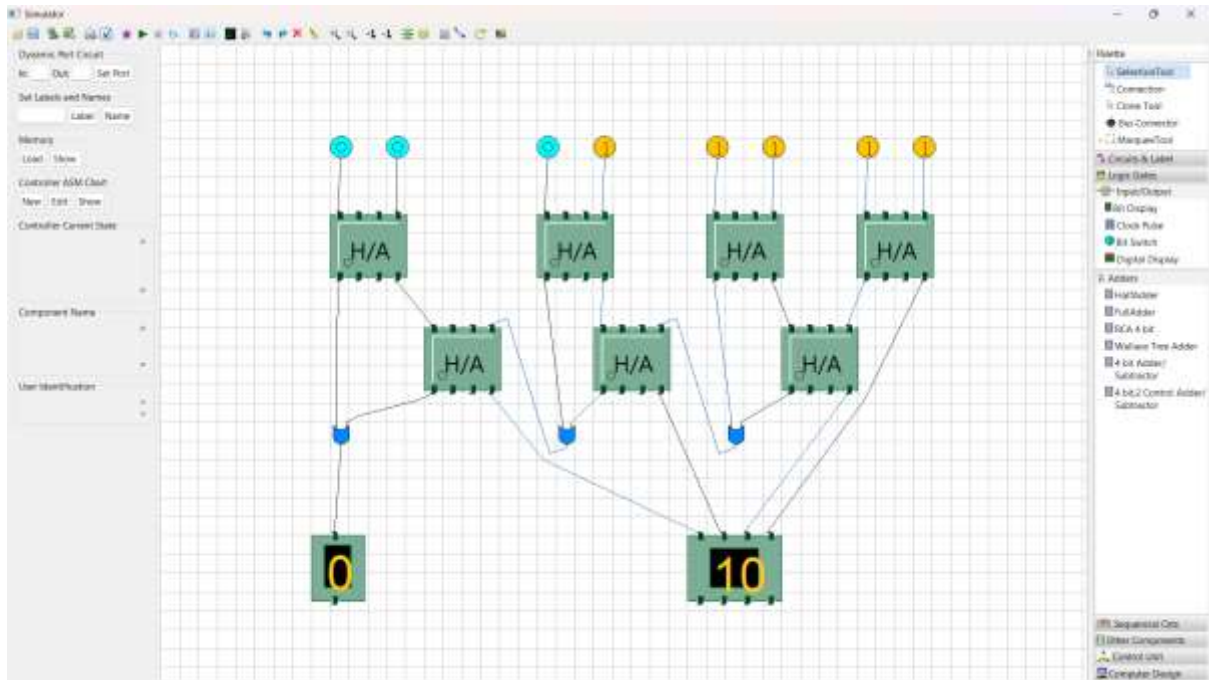

Conclusion:

The aim of the experiment is to design and implement a carry look-ahead adder, a high-speed digital arithmetic circuit that computes carry signals in parallel, enhancing addition efficiency and reducing propagation delays



Experiment No. 7
Implement Booth's algorithm using c-programming
Name: Ketan Mahadik
Roll Number: 24
Date of Performance:
Date of Submission:

Aim: To implement Booth's algorithm using c-programming.

Objective -


1. To understand the working of Booths algorithm.
2. To understand how to implement Booth's algorithm using c-programming.

Theory:

Booth's algorithm is a multiplication algorithm that multiplies two signed binary numbers in 2's complement notation. Booth used desk calculators that were faster at shifting than adding and created the algorithm to increase their speed.

The algorithm works as per the following conditions :

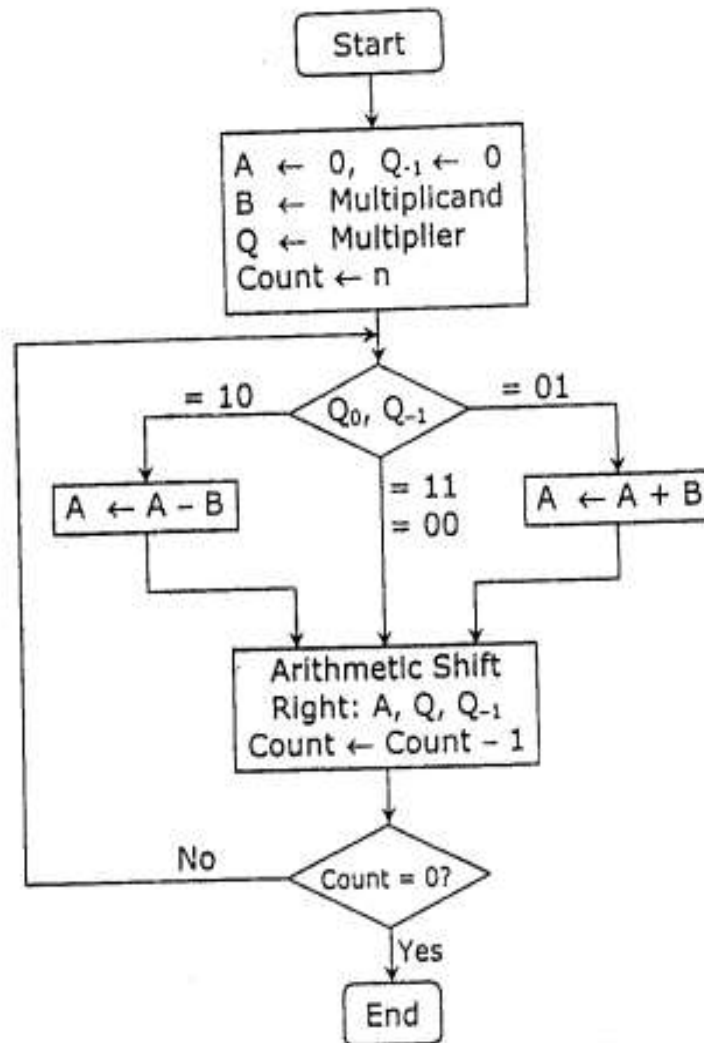1. If Q_n and Q_{-1} are same i.e. 00 or 11 perform arithmetic shift by 1 bit.
2. If $Q_n Q_{-1} = 10$ do $A = A - B$ and perform arithmetic shift by 1 bit.
3. If $Q_n Q_{-1} = 01$ do $A = A + B$ and perform arithmetic shift by 1 bit.



Multiplicand (B) ← 0 1 0 1 (5), Multiplier (Q) ← 0 1 0 0 (4)				
Steps	A	Q	Q ₋₁	Operation
	0 0 0 0	0 1 0 0	0	Initial
Step 1 :	0 0 0 0	0 0 1 0	0	Shift right
Step 2 :	0 0 0 0	0 0 0 1	0	Shift right
Step 3 :	1 0 1 1	0 0 0 1	0	A ← A - B
	1 1 0 1	1 0 0 0	1	Shift right
Step 4 :	0 0 1 0	1 0 0 0	1	A ← A + B
	0 0 0 1	0 1 0 0	0	Shift right
Result	0 0 0 1 0 1 0 0 = +20			

Program:



```
#include <stdio.h>
```

```
#include <math.h>
```

```
int a = 0, b = 0, c = 0, a1 = 0, b1 = 0, com[5] = { 1, 0, 0, 0, 0};
```

```
int anum[5] = {0}, anumcp[5] = {0}, bnum[5] = {0};
```

```
int acomp[5] = {0}, bcomp[5] = {0}, pro[5] = {0}, res[5] = {0};
```

```
void binary(){
```

```
    a1 = fabs(a);
```

```
    b1 = fabs(b);
```

```
    int r, r2, i, temp;
```

```
    for (i = 0; i < 5; i++){
```

```
        r = a1 % 2;
```

```
        a1 = a1 / 2;
```

```
        r2 = b1 % 2;
```

```
        b1 = b1 / 2;
```

```
        anum[i] = r;
```

```
        anumcp[i] = r;
```

```
        bnum[i] = r2;
```

```
        if(r2 == 0){
```

```
            bcomp[i] = 1;
```

```
        }
```

```
        if(r == 0){
```

```
            acomp[i] = 1;
```



```
}  
  
}  
  
//part for two's complementing  
  
c = 0;  
  
for ( i = 0; i < 5; i++){  
    res[i] = com[i]+ bcomp[i] + c;  
  
    if(res[i] >= 2){  
        c = 1;  
    }  
  
    else  
        c = 0;  
  
    res[i] = res[i] % 2;  
}  
  
for (i = 4; i >= 0; i--){  
    bcomp[i] = res[i];  
}  
  
//in case of negative inputs  
  
if (a < 0){  
    c = 0;  
  
    for (i = 4; i >= 0; i--){  
        res[i] = 0;  
    }  
  
    for ( i = 0; i < 5; i++){
```



```
res[i] = com[i] + acomp[i] + c;

if (res[i] >= 2){

    c = 1;

}

else

    c = 0;

res[i] = res[i]%2;

}

for (i = 4; i >= 0; i--){

    anum[i] = res[i];

    anumcp[i] = res[i];

}

}

if(b < 0){

    for (i = 0; i < 5; i++){

        temp = bnum[i];

        bnum[i] = bcomp[i];

        bcomp[i] = temp;

    }

}

}

void add(int num[]){
```



```
int i;

c = 0;

for ( i = 0; i < 5; i++){

    res[i] = pro[i] + num[i] + c;

    if (res[i] >= 2){

        c = 1;

    }

    else{

        c = 0;

    }

    res[i] = res[i]%2;

}

for (i = 4; i >= 0; i--){

    pro[i] = res[i];

    printf("%d",pro[i]);

}

printf(":");

for (i = 4; i >= 0; i--){

    printf("%d", anumcp[i]);

}

}

void arshift(){//for arithmetic shift right

    int temp = pro[4], temp2 = pro[0], i;
```



```
for (i = 1; i < 5 ; i++){//shift the MSB of product

    pro[i-1] = pro[i];

}

pro[4] = temp;

for (i = 1; i < 5 ; i++){//shift the LSB of product

    anumcp[i-1] = anumcp[i];

}

anumcp[4] = temp2;

printf("\nAR-SHIFT: ");//display together

for (i = 4; i >= 0; i--){

    printf("%d",pro[i]);

}

printf(":");

for(i = 4; i >= 0; i--){

    printf("%d", anumcp[i]);

}

}
```

```
void main(){

    int i, q = 0;

    printf("\t\tBOOTH'S MULTIPLICATION ALGORITHM");

    printf("\nEnter two numbers to multiply: ");

    printf("\nBoth must be less than 16");

}
```



```
//simulating for two numbers each below 16
```

```
do{
```

```
    printf("\nEnter A: ");
```

```
    scanf("%d",&a);
```

```
    printf("Enter B: ");
```

```
    scanf("%d", &b);
```

```
}while(a >=16 || b >=16);
```

```
printf("\nExpected product = %d", a * b);
```

```
binary();
```

```
printf("\n\nBinary Equivalents are: ");
```

```
printf("\nA = ");
```

```
for (i = 4; i >= 0; i--){
```

```
    printf("%d", anum[i]);
```

```
}
```

```
printf("\nB = ");
```

```
for (i = 4; i >= 0; i--){
```

```
    printf("%d", bnum[i]);
```

```
}
```

```
printf("\nB'+ 1 = ");
```

```
for (i = 4; i >= 0; i--){
```

```
    printf("%d", bcomp[i]);
```

```
}
```




```
printf("\n\n");

for (i = 0; i < 5; i++){

    if (anum[i] == q){//just shift for 00 or 11

        printf("\n-->");

        arshift();

        q = anum[i];

    }

    else if(anum[i] == 1 && q == 0){//subtract and shift for 10

        printf("\n-->");

        printf("\nSUB B: ");

        add(bcomp);//add two's complement to implement subtraction

        arshift();

        q = anum[i];

    }

    else{//add ans shift for 01

        printf("\n-->");

        printf("\nADD B: ");

        add(bnum);

        arshift();

        q = anum[i];

    }

}
```



```
printf("\nProduct is = ");  
  
for (i = 4; i >= 0; i--){  
    printf("%d", pro[i]);  
  
}  
  
for (i = 4; i >= 0; i--){  
    printf("%d", anumcp[i]);  
  
}  
  
}
```

Output:



```
Both must be less than 16
Enter A: 2
Enter B: 4
Expected product = 8

Binary Equivalents are:
A = 00010
B = 00100
B' + 1 = 11100

-->
AR-SHIFT: 00000:00001
-->
SUB B: 11100:00001
AR-SHIFT: 11110:00000
-->
ADD B: 00010:00000
AR-SHIFT: 00001:00000
-->
```

Conclusion - The aim of the experiment is to implement Booth's algorithm in C programming, a multiplication algorithm that efficiently and effectively multiplies two binary numbers using a sequential approach, reducing the number of partial products and improving computational speed.

Experiment No. 8
Implement Restoring algorithm using c-programming
Name: ketan mahadik
Roll Number: 24
Date of Performance:
Date of Submission:

Aim: To implement Restoring division algorithm using c-programming.



Objective -

1. To understand the working of Restoring division algorithm.
2. To understand how to implement Restoring division algorithm using c-programming.

Theory:


- 1) The divisor is placed in M register, the dividend placed in Q register.
- 2) At every step, the A and Q registers together are shifted to the left by 1-bit
- 3) M is subtracted from A to determine whether A divides the partial remainder. If it does, then Q0 set to 1-bit. Otherwise, Q0 gets a 0 bit and M must be added back to A to restore the previous value.
- 4) The count is then decremented and the process continues for n steps. At the end, the quotient is in the Q register and the remainder is in the A register.

Flowchart



Vidyavardhini's College of Engineering & Technology

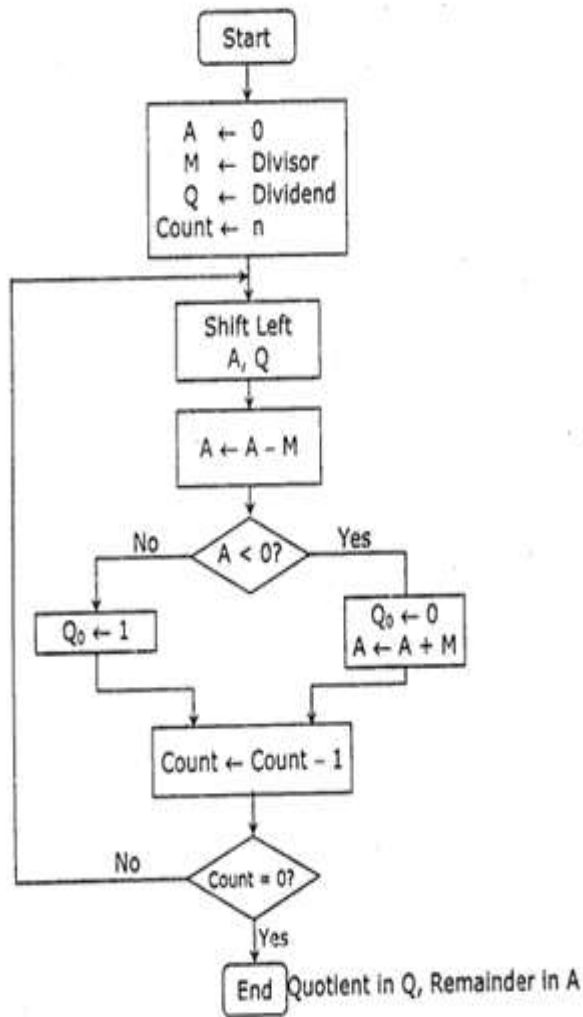Department of Artificial Intelligence and Data Science



Perform $8 \div 3$ by restoring division technique.

	A Register	Q Register	
Initially	0 0 0 0 0	1 0 0 0	First Cycle
Shift	0 0 0 0 1	0 0 0 □	
Subtract M	1 1 1 0 1		
Set Q₀	① 1 1 1 0		
Restore(A+M)	0 0 0 1 1	0 0 0 □	Second Cycle
Shift	0 0 0 1 0	0 0 □ □	
Subtract M	1 1 1 0 1		
Set Q₀	① 1 1 1 1		
Restore(A+M)	0 0 0 1 1	0 0 □ □	Third Cycle
Shift	0 0 1 0 0	0 □ □ □	
Subtract M	1 1 1 0 1		
Set Q₀	① 0 0 0 1		
Shift	0 0 0 1 0	0 0 □ □	Fourth Cycle
Subtract M	1 1 1 0 1	□ □ □ □	
Set Q₀	① 1 1 1 1		
Restore(A+M)	0 0 0 1 1	□ □ □ □	
	0 0 0 1 0	□ □ □ □	
	Remainder	Quotient	

Program-

```
#include <stdio.h>
```

```
#include <stdlib.h>
```

```
int dec_bin(int, int []);
```

```
int twos(int [], int []);
```

```
int left(int [], int []);
```

```
int add(int [], int []);
```



```
int main()
{
    int a, b, m[4]={0,0,0,0}, q[4]={0,0,0,0}, acc[4]={0,0,0,0}, m2[4], i, n=4;

    printf("Enter the Dividend: ");

    scanf("%d", &a);

    printf("Enter the Divisor: ");

    scanf("%d", &b);

    dec_bin(a, q);

    dec_bin(b, m);

    twos(m, m2);

    printf("\nA\tQ\tComments\n");

    for(i=3; i>=0; i--)
    {
        printf("%d", acc[i]);
    }

    printf("\t");

    for(i=3; i>=0; i--)
    {
        printf("%d", q[i]);
    }

    printf("\tStart\n");

    while(n>0)
    {
```



```
left(acc, q);

for(i=3; i>=0; i--)

{

    printf("%d", acc[i]);

}

printf("\t");

for(i=3; i>=1; i--)

{

    printf("%d", q[i]);

}

printf("_\tLeft Shift A,Q\n");

add(acc, m2);

for(i=3; i>=0; i--)

{

    printf("%d", acc[i]);

}

printf("\t");

for(i=3; i>=1; i--)

{

    printf("%d", q[i]);

}

printf("_\tA=A-M\n");

if(acc[3]==0)
```




```
{  
    q[0]=1;  
    for(i=3; i>=0; i--)  
    {  
        printf("%d", acc[i]);  
    }  
    printf("\t");  
    for(i=3; i>=0; i--)  
    {  
        printf("%d", q[i]);  
    }  
    printf("\tQo=1\n");  
}  
else  
{  
    q[0]=0;  
    add(acc, m);  
    for(i=3; i>=0; i--)  
    {  
        printf("%d", acc[i]);  
    }  
    printf("\t");  
    for(i=3; i>=0; i--)
```



```
{  
    printf("%d", q[i]);  
}  
  
printf("\tQo=0; A=A+M\n");  
  
}  
  
n--;  
  
}  
  
printf("\nQuotient = ");  
  
for(i=3; i>=0; i--)  
{  
    printf("%d", q[i]);  
}  
  
printf("\tRemainder = ");  
  
for(i=3; i>=0; i--)  
{  
    printf("%d", acc[i]);  
}  
  
printf("\n");  
  
return 0;  
}
```

```
int dec_bin(int d, int m[])
```

```
{
```



```
int b=0, i=0;

for(i=0; i<4; i++)

{

    m[i]=d%2;

    d=d/2;

}

return 0;

}

int twos(int m[], int m2[])

{

    int i, m1[4];

    for(i=0; i<4; i++)

    {

        if(m[i]==0)

        {

            m1[i]=1;

        }

        else

        {

            m1[i]=0;

        }

    }

}
```



```
for(i=0; i<4; i++)
```

```
{
```

```
    m2[i]=m1[i];
```

```
}
```

```
if(m2[0]==0)
```

```
{
```

```
    m2[0]=1;
```

```
}
```

```
else
```

```
{
```

```
    m2[0]=0;
```

```
    if(m2[1]==0)
```

```
    {
```

```
        m2[1]=1;
```

```
    }
```

```
else
```

```
{
```

```
    m2[1]=0;
```

```
    if(m2[2]==0)
```

```
    {
```

```
        m2[2]=1;
```

```
    }
```

```
else
```



```
{  
    m2[2]=0;  
    if(m2[3]==0)  
    {  
        m2[3]=1;  
    }  
    else  
    {  
        m2[3]=0;  
    }  
}  
}  
}  
return 0;  
}
```

```
+int left(int acc[], int q[])  
{  
    int i;  
    for(i=3; i>0; i--)  
    {  
        acc[i]=acc[i-1];  
    }  
}
```



```
acc[0]=q[3];

for(i=3; i>0; i--)

{

    q[i]=q[i-1];

}

}

int add(int acc[], int m[])

{

    int i, carry=0;

    for(i=0; i<4; i++)

    {

        if(acc[i]+m[i]+carry==0)

        {

            acc[i]=0;

            carry=0;

        }

        else if(acc[i]+m[i]+carry==1)

        {

            acc[i]=1;

            carry=0;

        }

        else if(acc[i]+m[i]+carry==2)
```



```
{  
    acc[i]=0;  
    carry=1;  
}  
else if(acc[i]+m[i]+carry==3)  
{  
    acc[i]=1;  
    carry=1;  
}  
}  
return 0;  
}
```

Output -



Terminal

Enter the Dividend: 15

Enter the Divisor: 5

A	Q	Comments
0000	1111	Start
0001	111_	Left Shift A,Q
1100	111_	A=A-M
0001	1110	Qo=0; A=A+M
0011	110_	Left Shift A,Q
1110	110_	A=A-M
0011	1100	Qo=0; A=A+M
0111	100_	Left Shift A,Q
0010	100_	A=A-M
0010	1001	Qo=1
0101	001_	Left Shift A,Q
0000	001_	A=A-M
0000	0011	Qo=1

Quotient = 0011 Remainder = 0000

Conclusion - - The aim of the experiment is to implement the Restoring division algorithm in C programming, a method for efficiently performing division by restoring partial remainders and quotients, aiming to optimize the division process and achieve accurate results in a systematic manner.



Experiment No. 9
Implement Non-Restoring algorithm using c-programming
Name: ketan mahadik
Roll Number: 24
Date of Performance:
Date of Submission:


Aim - To implement Non-Restoring division algorithm using c-programming.

Objective -

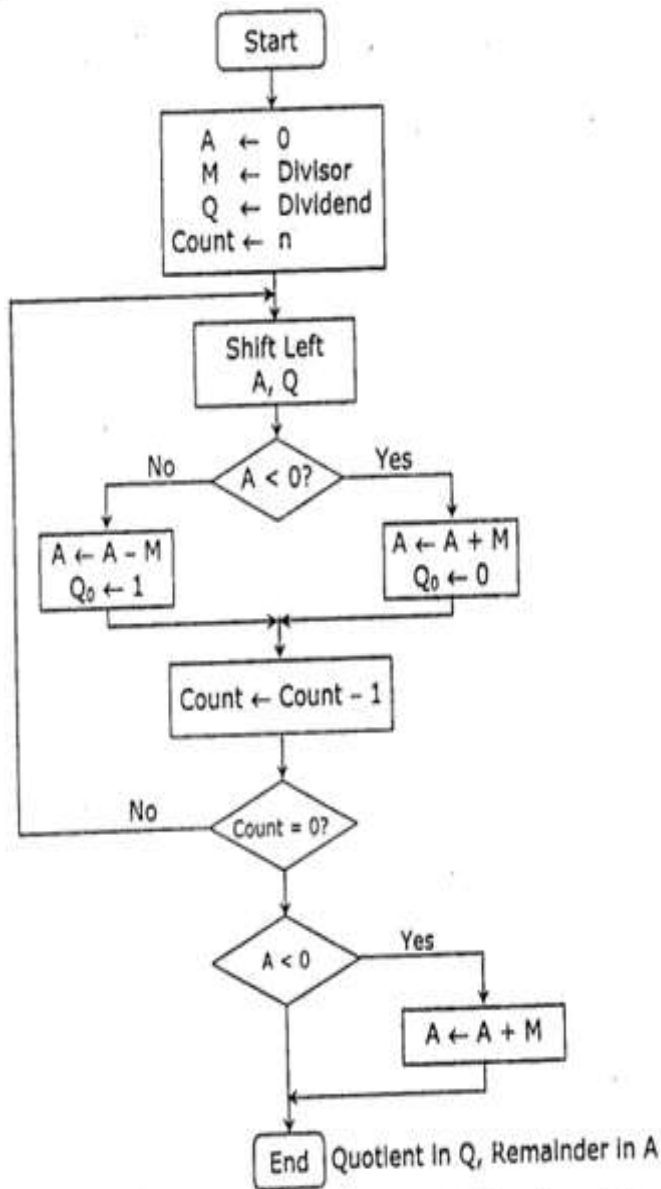1. To understand the working of Non-Restoring division algorithm.
2. To understand how to implement Non-Restoring division algorithm using c-programming.

Theory:

In each cycle content of the register, A is first shifted and then the divisor is added or subtracted with the content of register A depending upon the sign of A. In this, there is no need of restoring, but if the remainder is negative then there is a need of restoring the remainder. This is the faster algorithm of division.



Perform $8 + 3$ by non-restoring division technique.

	A Register	Q Register	
Initially	0 0 0 0	1 0 0 0	
Shift	0 0 0 0 1	0 0 0 □	
Subtract	1 1 1 0 1		
Set Q_0	① 1 1 1 0	0 0 0 ①	First Cycle
Shift	1 1 1 0 0	0 0 ① □	
Add	0 0 0 1 1		
Set Q_0	① 1 1 1 1	0 0 ① ①	Second Cycle
Shift	1 1 1 1 0	0 ① ① □	
Add	0 0 0 1 1		
Set Q_0	① 0 0 0 1	0 0 ① ①	Third Cycle
Shift	0 0 0 1 0	0 ① ① □	
Subtract	1 1 1 0 1		
Set Q_0	① 1 1 1 1	0 0 ① ①	Fourth Cycle
Add	1 1 1 1 1		Quotient
	0 0 0 1 1		
	0 0 0 1 0		Remainder



Program -

```
#include <math.h>

#include <stdio.h>

//NON RESTORING DIVISION

int main()
{
    int a[50],a1[50],b[50],d=0,i,j;

    int n1,n2, c, k1,k2,n,k,quo=0,rem=0;

    printf("Enter the number of bits\n");

    scanf("%d",&n);

    printf("Enter the divisor and dividend\n");

    scanf("%d %d", &n1,&n2);

    for (c = n-1; c >= 0; c--)//converting the 2 nos to binary
    {
        k1 = n1 >> c;

        if (k1 & 1)

            a[n-1-c]=1;// M

        else

            a[n-1-c]=0;

        k2 = n2 >> c;
```



```
if (k2 & 1)
```

```
    b[2*n-1-c]=1;// Q
```

```
else
```

```
    b[2*n-1-c]=0;
```

```
}
```

```
for(i=0;i<n;i++)//making complement
```

```
{
```

```
    if(a[i]==0)
```

```
        a1[i]=1;
```

```
    else
```

```
        a1[i]=0;
```

```
}
```

```
a1[n-1]+=1;//twos complement ie -M
```

```
if(a1[n-1]==2)
```

```
{
```

```
    for(i=n-1;i>0;i--)
```

```
    {
```

```
        if(a1[i]==2)
```



```
{  
    a1[i-1]+=1;  
    a1[i]=0;  
}  
}  
}  
  
if(a1[0]==2)  
    a1[0]=0;  
  
for( i=0;i<n;i++)// putting A in the same array as Q  
{  
    b[i]=0;  
  
}  
  
printf("A\tQ\tPROCESS\n");  
  
for(i=0;i<2*n;i++)  
{  
    if(i==n)  
        printf("\t");  
  
    printf("%d",b[i]);  
  
}
```



```
}
```

```
printf("\n");
```

```
for(k=0;k<n;k++)//n iterations
```

```
{
```

```
for(j=0;j<2*n-1;j++)//left shift
```

```
{
```

```
    b[j]=b[j+1];
```

```
}
```

```
for(i=0;i<2*n-1;i++)
```

```
{
```

```
    if(i==n)
```

```
        printf("\t");
```

```
        printf("%d",b[i]);
```

```
    }printf("_ ");
```

```
printf("\tLEFT SHIFT\n");
```

```
if(b[0]==0)
```

```
{
```

```
    for(i=n-1;i>=0;i--)//A=A-M
```



Vidyavardhini's College of Engineering & Technology

Department of Artificial Intelligence and Data Science

```
{  
    b[i]+=a1[i];  
  
    if(i!=0)  
    {  
        if(b[i]==2)  
        {  
            b[i-1]+=1;  
            b[i]=0;  
        }  
        if(b[i]==3)  
        {  
            b[i-1]+=1;  
            b[i]=1;  
        }  
        // printf("%d",b[i]);  
    }  
}  
  
if(b[0]==2)  
    b[0]=0;  
  
if(b[0]==3)  
    b[0]=1;
```




```
for(i=0;i<2*n -1;i++)  
  
    {  
  
        if(i==n)  
  
            printf("\t");  
  
  
  
  
            printf("%d",b[i]);  
  
        }printf("_");  
  
  
        printf("\tA-M\n");  
  
    }  
  
else  
  
    {  
  
        for(j=n-1;j>=0;j--)//A=A+M  
  
            {  
  
                b[j]+=a[j];  
  
  
  
                if(j!=0)  
  
                    {  
  
                        if(b[j]==2)
```



```
{  
    b[j-1]+=1;  
    b[j]=0;  
}  
if(b[j]==3)  
{  
    b[j-1]+=1;  
    b[j]=1;  
}  
}  
  
if(b[0]==2)  
    b[0]=0;  
  
if(b[0]==3)  
    b[0]=1;  
}  
  
for(i=0;i<2*n-1;i++)  
{  
    if(i==n)  
        printf("\t");
```



Vidyavardhini's College of Engineering & Technology

Department of Artificial Intelligence and Data Science

```
        printf("%d",b[i]);  
  
    }printf("_");  
  
    printf("\tA+M\n");  
  
}
```

```
if(b[0]==0)//A==0?  
{  
    b[2*n-1]=1;  
    for(i=0;i<2*n;i++)  
    {  
        if(i==n)  
            printf("\t");
```

```
        printf("%d",b[i]);  
    }
```



```
printf("\tQ0=1\n");  
}
```

```
if(b[0]==1)//A==1?  
{  
    b[2*n-1]=0;  
    for(i=0;i<2*n;i++)  
    {  
        if(i==n)  
            printf("\t");
```

```
        printf("%d",b[i]);  
    }
```

```
    printf("\tQ0=0\n");  
  
}
```



```
}
```

```
if(b[0]==1)
```

```
{
```

```
    for(j=n-1;j>=0;j--)//A=A+M
```

```
    {
```

```
        b[j]+=a[j];
```

```
        if(j!=0)
```

```
    {
```

```
        if(b[j]==2)
```

```
        {
```

```
            b[j-1]+=1;
```

```
            b[j]=0;
```

```
        }
```

```
        if(b[j]==3)
```

```
        {
```

```
            b[j-1]+=1;
```

```
            b[j]=1;
```

```
        }
```

```
    }
```

```
    if(b[0]==2)
```



```
b[0]=0;
```

```
if(b[0]==3)
```

```
    b[0]=1;
```

```
}
```

```
for(i=0;i<2*n;i++)
```

```
{
```

```
    if(i==n)
```

```
        printf("\t");
```

```
        printf("%d",b[i]);
```

```
    }
```

```
    printf("\tA+M\n");
```

```
}
```

```
printf("\n");
```

```
for(i=n;i<2*n;i++)
```

```
{
```

```
    quo+= b[i]*pow(2,2*n-1-i);
```

```
}
```



```
for(i=0;i<n;i++)  
{  
    rem+= b[i]*pow(2,n-1-i);  
}  
  
printf("The quotient of the two nos is %d\nThe remainder is %d",quo,rem);  
  
printf("\n");  
  
return 0;  
}
```

Output:

```
5  
4  
A   Q   PROCESS  
0000 0100  
0000 100_  LEFT SHIFT  
1011 100_  A-M  
1011 1000  Q0=0  
0111 000_  LEFT SHIFT  
0010 000_  A-M  
0010 0001  Q0=1  
0100 001_  LEFT SHIFT  
1111 001_  A-M  
1111 0010  Q0=0  
1110 010_  LEFT SHIFT  
0011 010_  A+M  
0011 0101  Q0=1  
  
The quotient of the two nos is 5  
The remainder is 3
```



Vidyavardhini's College of Engineering & Technology

Department of Artificial Intelligence and Data Science

Conclusion -- The aim of the experiment is to implement the Non-Restoring division algorithm in C programming, a technique for efficient division that avoids restoring partial remainders, aiming to streamline the division process and achieve precise results through a systematic approach.



Experiment No.10
Implement ALU design.
Name: ketan mahadik
Roll Number: 24
Date of Performance:
Date of Submission:


Aim: To implement ALU design

Objective : Objective of 4 bit arithmetic logic unit (with AND, OR, XOR, ADD operation):

1. To understand behaviour of arithmetic logic unit from working module.
2. To Design an arithmetic logic unit for given parameter.

Theory:

ALU or Arithmetic Logical Unit is a digital circuit to do arithmetic operations like addition, subtraction, division, multiplication and logical operations like and, or, xor, nand, nor etc. A simple block diagram of a 4 bit ALU for operations and, or, xor and Add is shown here :

 

The 4-bit ALU block is combined using 4 1-bit ALU block

Design Issues :



Vidyavardhini's College of Engineering & Technology

Department of Artificial Intelligence and Data Science

The circuit functionality of a 1 bit ALU is shown here, depending upon the control signal S1 and S0 the circuit operates as follows:

for Control signal S1 = 0 , S0 = 0, the output is A And B,

for Control signal S1 = 0 , S0 = 1, the output is A Or B,

for Control signal S1 = 1 , S0 = 0, the output is A Xor B,

for Control signal S1 = 1 , S0 = 1, the output is A Add B.

The truth table for 16-bit ALU with capabilities similar to 74181 is shown here:

Required functionality of ALU (inputs and outputs are active high)

MODE SELECT	F _N FOR ACTIVE HIGH OPERANDS	
INPUTS	LOGIC	ARITHMETIC (NOTE 2)

S3	S2	S1	S0	(M = H)	(M = L) (Cn=L)
L	L	L	L	A'	A
L	L	L	H	A'+B'	A+B
L	L	H	L	A'B	A+B'
L	L	H	H	Logic 0	minus 1
L	H	L	L	(AB)'	A plus AB'
L	H	L	H	B'	(A + B) plus AB'
L	H	H	L	$A \oplus B$	A minus B minus 1
L	H	H	H	AB'	AB minus 1
H	L	L	L	A'+B	A plus AB
H	L	L	H	$(A \oplus B)'$	A plus B
H	L	H	L	B	(A + B') plus AB
H	L	H	H	AB	AB minus 1
H	H	L	L	Logic 1	A plus A (Note 1)
H	H	L	H	A+B'	(A + B) plus A
H	H	H	L	A+B	(A + B') plus A
H	H	H	H	A	A minus 1

Procedure


- 1) Start the simulator as directed. This simulator supports 5-valued logic.
- 2) To design the circuit we need 4 1-bit ALU, 11 Bit switch (to give input, which will toggle its value with a double click), 5 Bit displays (for seeing output), wires.
- 3) The pin configuration of a component is shown whenever the mouse is hovered on any canned component of the palette. Pin numbering starts from 1 and from the bottom left corner (indicating with the circle) and increases anticlockwise.
- 4) For 1-bit ALU input A0 is in pin-9, B0 is in pin-10, C0 is in pin-11 (this is input carry), for selection of operation, S0 is in pin-12, S1 is in pin-13, output F is in pin-8 and output carry is pin-7
- 5) Click on the 1-bit ALU component (in the Other Component drawer in the pallet) and then click on the position of the editor window where you want to add the component



(no drag and drop, simple click will serve the purpose), likewise add 3 more 1-bit ALU (from the Other Component drawer in the pallet), 11 Bit switches and 5 Bit Displays (from Display and Input drawer of the pallet, if it is not seen scroll down in the drawer), 3 digital display and 1 bit Displays (from Display and Input drawer of the pallet, if it is not seen scroll down in the drawer)

- 6) To connect any two components select the Connection menu of Palette, and then click on the Source terminal and click on the target terminal. According to the circuit diagram connect all the components. Connect the Bit switches with the inputs and Bit displays component with the outputs. After the connection is over click the selection tool in the pallet.
- 7) See the output, in the screenshot diagram we have given the value of S1 S0=11 which will perform add operation and two number input as A0 A1 A2 A3=0010 and B0 B1 B2 B3=0100 so get output F0 F1 F2 F3=0110 as sum and 0 as carry which is indeed an add operation. you can also use many other combination of different values and check the result. The operations are implemented using the truth table for 4 bit ALU given in the theory.

Circuit diagram of 4 bit ALU:

 

Components required :

To build any 4 bit ALU, we need :


- AND gate, OR gate, XOR gate
- Full Adder,
- 4-to-1 MUX
- Wires to connect.

Screenshots of ALU design:



Vidyavardhini's College of Engineering & Technology

 Department of Artificial Intelligence and Data Science



Conclusion: The aim of the experiment is to design and implement an Arithmetic Logic Unit (ALU) in order to perform arithmetic and logic operations on binary data, with a focus on optimizing speed, efficiency, and versatility in digital computing systems